

I - ASSIGNMENT

(Start Writing From Here)


1 How to implement NOT, AND and OR gate using NAND and NOR gates.

i) Implementing AND, OR, NOT gates using NAND


i) NOT by using NAND



ii) AND by using NAND

 


iii) OR by using NAND

 

2) Implementing AND, OR, NOT by using NOR gate

i) AND by using NOR

 

ii) OR gate by using NOR



iii) NOT gate by using NOR



2. Find out sop for the following

A) $F(A, B, C) = AB + BC'$

B) $F(A, B, C, D) = A + B'CD'$

A) $F(A, B, C) = AB + BC'$

$$AB(C' + C) + (A' + A)BC'$$

$$ABC' + ABC + A'BC' + ABC'$$

$$\begin{matrix} 110 & 111 & 010 & 110 \end{matrix}$$

$$\begin{matrix} m_6 & m_7 & m_2 & m_6 \end{matrix}$$

$$\therefore \begin{cases} C' + C = 1 \\ A' + A = 1 \end{cases}$$

\therefore This is sop form of given equation.

B) $F(A, B, C, D) = A + B'CD'$

$$A(B' + B) + B'CD'(A' + A)$$

$$AB' + AB + A'B'CD' + AB'CD'$$

$$AB'(C' + C) + AB(C' + C) + A'B'CD' + AB'CD'$$

(4)

$$\begin{aligned}
 &= AB'C' + AB'C + ABC' + ABC + A'B'C'D' + AB'CD' \\
 &= AB'C'(D'+D) + AB'C(D'+D) + ABC'(D'+D) + ABC(D'+D) \\
 &\quad + A'B'C'D' + AB'CD' \\
 &= AB'C'D' + AB'C'D + AB'CD' + AB'CD + ABC'D' + ABC'D \\
 &\quad + ABCD' + ABCD + A'B'C'D' + AB'CD'
 \end{aligned}$$

∴ This is SOP form for given $f(A, B, C, D)$

3. Demonstrate the design steps of synchronous counters with suitable examples?

Design of synchronous counter

A synchronous counter is a type of counter in which all the flip flops are triggered simultaneously by the same clock pulse.

step 1 :- Determine the number of flip-flops required.

Firstly, analyze the problem description and determine the number of flip-flops required to implement the synchronous counter. If n is the required number of flip flops, then the smallest value of n is such that the number of states N is less than or equal to 2^n .

step 2:- Draw the state diagram.

Secondly, draw the state diagram that shows all the possible states. The state diagram is basically a graphical way of representing the sequence of states through which the counter progress. In the state diagram, we can also include the case in which the counter goes to a particular state from the invalid states on the next clock pulse.

step 3:- selection of flip-flops and excitation table.

In the third step, select a particular type of flip-flop to be used to implement the counter and draw its excitation table. The excitation table is one that gives the information about the present states, next states, and required excitation of the flip-flop.

step 4:- obtain the minimized expression for excitation

Now, obtain the minimal expressions for the excitations of the flipflops by using any minimization technique such as K-map.

step 5:- draw the logic diagram

Draw the logic circuit diagram according to the minimal expression obtained in the step 4.

Example:

Design a synchronous counter using D flip flops that goes through states 0, 1, 2, 4, 0. The unused states must always go to zero on the next clock pulse.

solution:-


step 1:- Number of Flip Flops required.

This synchronous counter has for stable states, i.e., 0(000), 1(100), 2(00), 4(100). But we require three flip flops because it counts 4(100) as well.

Since three flip-flops can count eight states. Thus, the remaining four states, i.e., 3(011), 5(101), 6(110) and 7(111) are unused states, the unused states must go to 0(000) after the next clock pulse.

step 2:- Draw the state diagram.

 The state diagram of the 0, 1, 2, 4, 0... counter.



state diagram

step 3:- choose the type of flip flop and write the excitation table.

Present state			Next state			Required Excitation		
Q_2	Q_1	Q_0	Q_2	Q_1	Q_0	D_2	D_1	D_0
0	0	0	0	0	1	0	0	1
0	0	1	0	1	0	0	1	0
0	1	0	1	0	0	1	0	0
0	1	1	0	0	0	0	0	0
1	0	0	0	0	0	0	0	0
1	0	1	0	0	0	0	0	0
1	1	0	0	0	0	0	0	0
1	1	1	0	0	0	0	0	0

step 4:- Derive the minimal expression


From the excitation table, we can see that there is no minimization is possible. Hence, the expressions for the excitation can be directly written from the excitation table itself as follows:-

$$D_1 = Q_3' Q_2' Q_1'$$

$$D_2 = Q_3' Q_2' Q_1'$$

$$D_3 = Q_3' Q_2' Q_1'$$

step 5:- Draw the logic circuit diagram.

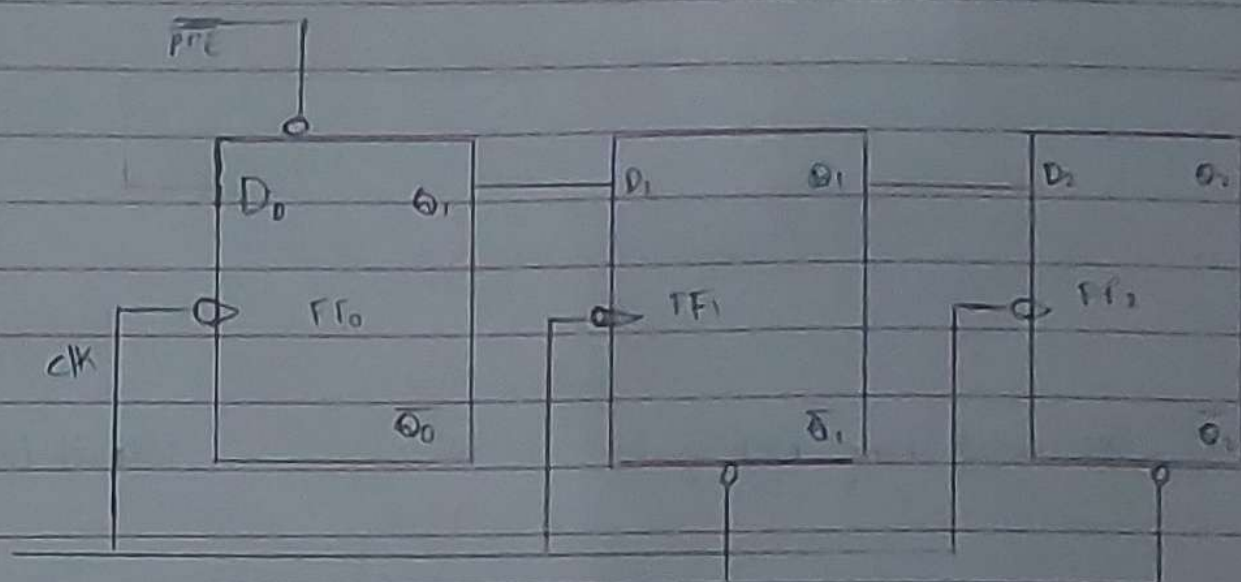

Logic circuit Diagram of Counter

- 4) Explain about S-R latch with a neat diagram using NAND and NOR gates

Ans → S-R latch:-


They are also known as present and clear states. The S-R latch forms the basic building blocks of all other types of flip-flops.

SP latch in a circuit with

- i) 2 cross-coupled NOR gate or 2 cross-coupled NAND gate
- ii) 2 input S for SET and R for RESET
- iii) 2 output Q, Q'

i) S-R Latch using NAND gates.


ii) Truth table.

 

S	R	Q	Q'
0	0	Invalid condition (not used)	
0	1	1	0
1	0	0	1
1	1	memory / hold state	

ii) R-Latch using NOR gates

ii) Truth table

 

S	R	Q	Q'
0	0	memory / hold state	
0	1	0	1
1	0	1	0
1	1	Invalid state (not used)	


5) What are the different types of Instruction codes?

Types of Instruction code.

In general, there are three codes formats for computer instructions of 16-bit code, the opcode usually contains 3 bits and the rest of 13-bit is subjective, depending on the operation code encountered.

 
1) memory-reference instruction:-

In this type of code, 12 bits are used to specify the operation memory address, 3 bits for the opcode (000 to 110), and 1 bit to specify the mode as indirect addressing mode (1)



 2) Register-reference instruction:-

12 bits indicate the register operation address, 3 bits for the opcode (111), and 1 bit is utilised for setting the mode as 0, the instructions are executed on the register



3) Input-output instruction:-

This type of code contains a 12-bit input/output operation address, 3 bits for the opcode (111) and 1 bit is utilised for setting the mode as 1.

These instructions are required to transfer to and from the AC register and output device

